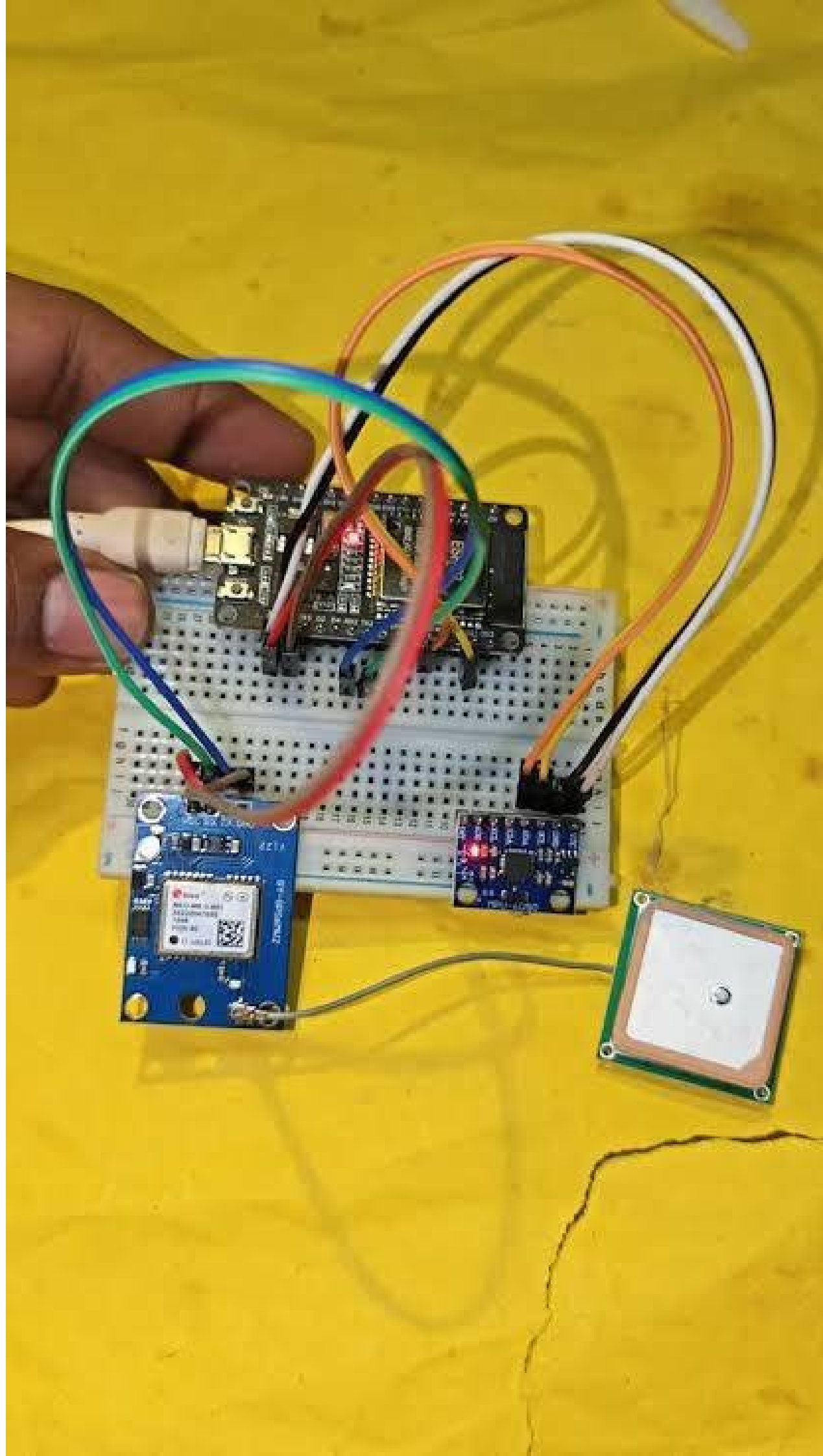
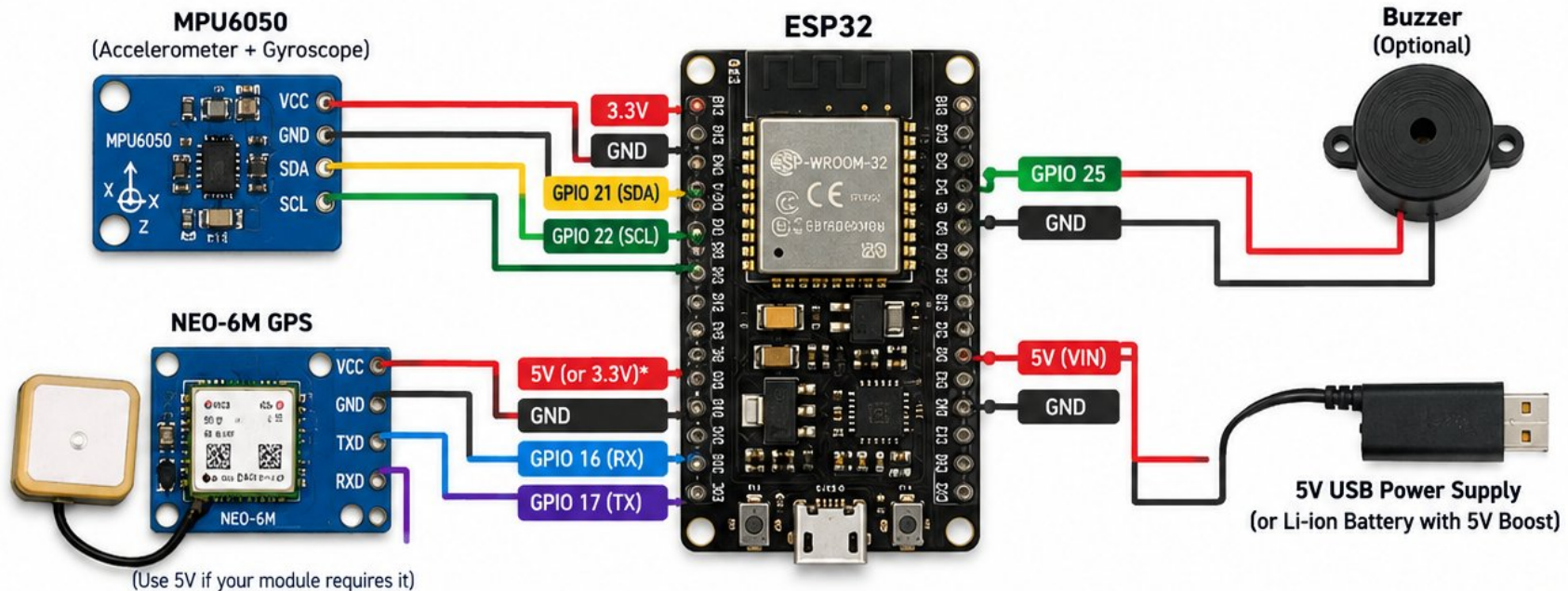




ESP32 Accident Detection & Alert System Circuit Diagram

(ESP32 + MPU6050 + NEO-6M GPS + Buzzer)



Pin Connections

Component	Component Pin	ESP32 Pin
MPU6050	VCC	3.3V
	GND	GND
	SDA	GPIO 21
	SCL	GPIO 22
NEO-6M GPS	VCC	5V (or 3.3V)*
	GND	GND
	TXD	GPIO 16 (RX)
	RXD	GPIO 17 (TX)
Buzzer	+	GPIO 25
	-	GND
Power Supply	5V (VIN)	5V (USB / Battery)
	GND	GND

Notes

- MPU6050 works on I2C (SDA & SCL).
- NEO-6M GPS uses UART (TX & RX).
- GPS module usually works on 5V. If your module supports 3.3V, you can use 3.3V from ESP32.
- Make sure to connect all GND pins together (common ground).
- Use a proper 5V power source (USB charger or power bank).
- Pin numbers may vary depending on your ESP32 board (e.g., DevKit V1, WROOM, etc.). Adjust according to your board documentation.
- Keep wires short and use a breadboard or PCB for a clean setup.

⚠ Important:

Do not connect both 5V and 3.3V to the same module. Use only the required voltage.

Wire Color Guide

- 5V / VCC (Power)
- GND (Ground)
- SDA (I2C)
- SCL (I2C)
- TX (UART)
- RX (UART)

System Flow

